



CSE112

## **Computer Organization and Architecture**

Submitted to

*Dr. Tamer Mostafa*

*Dr. Karim Emara*

*Eng. Yasmin Shaaban*

# Major Task Report

## Team 8 Members

Name	ID
Mohamed Hany Mohamed Fadel	21P0299
Mazen Ahmed Galal	21P0103
Hams Assem Ahmed	20P3713
Bassel Ashraf	22P0122
Ezzeldine Ahmed Ali	21P0078

# Table of Contents

<b>Top module.....</b>	<b>7</b>
1.Code .....	7
2.RTL.....	8
3. Explanation .....	9
<b>MIPS .....</b>	<b>10</b>
1.Code .....	10
2.RTL.....	11
3.Explanation .....	12
<b>IMEM.....</b>	<b>13</b>
1.Code .....	13
2.RTL.....	15
3.Explanation .....	16
<b>DMEM .....</b>	<b>17</b>
1.Code .....	17
2.RTL.....	18
3.Explanation .....	18
<b>Controller .....</b>	<b>19</b>
1.Code .....	19
2.RTL.....	20
3. Explanation .....	21
<b>Main Decoder .....</b>	<b>22</b>
1.Code .....	22
2.RTL.....	24
3.Explanation .....	25
<b>ALU Decoder .....</b>	<b>26</b>
1.Code .....	26

2.RTL.....	27
3.Explanation .....	28
<b>Data Path .....</b>	<b>29</b>
1.Code .....	29
2.RTL.....	33
3.Explanation .....	33
<b>Register File .....</b>	<b>34</b>
1.Code .....	34
2.RTL.....	40
3.Explanation .....	43
<b>ALU .....</b>	<b>44</b>
1.Code .....	44
2.RTL.....	45
3.Explanation .....	48
<b>Mux 2*1.....</b>	<b>49</b>
1.Code .....	49
<b>Mux 32*1.....</b>	<b>50</b>
1.Code .....	50
2.RTL.....	53
<b>Flopr .....</b>	<b>54</b>
1.Code .....	54
2.RTL.....	55
<b>Decoder .....</b>	<b>56</b>
1.Code .....	56
2.RTL.....	58
<b>Adder.....</b>	<b>59</b>
1.Code .....	59

2.RTL.....	60
<b>Sign Extender.....</b>	<b>61</b>
1.Code .....	61
2.RTL.....	61
<b>Shift left 2 .....</b>	<b>62</b>
1.Code .....	62
2.RTL.....	62
<b>Test Files .....</b>	<b>63</b>
<b>Main Module Test .....</b>	<b>63</b>
1.Code .....	63
2.Test Results .....	65



# Top module

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use work.Mips_Package.all;
```

```
use work.Dmem_Package.all;
```

```
use work.Imem_Package.all;
```

```
entity TopModule is
```

```
    Port ( clk : in  STD_LOGIC;
```

```
          rst : in  STD_LOGIC;
```

```
          writedata : out  STD_LOGIC_VECTOR (31 downto 0);
```

```
          dataadr : out  STD_LOGIC_VECTOR (31 downto 0);
```

```
          memwrite : out  STD_LOGIC);
```

```
end TopModule;
```

```
architecture Behavioral of TopModule is
```

```
    signal memwritet: STD_LOGIC;
```

```
    signal PC,instr,readdata,dataadrt,writedatat: STD_LOGIC_VECTOR (31 downto 0);
```

```
begin
```

```
InstructionMemory: imem port map(pc(7 downto 2),instr);
```

```
MipsMap: Mips port
```

```
map(clk,rst,pc,instr,memwritet,dataadrt,writedatat,readdata);
```

```
DataMemory: dmem port map(clk,memwritet,dataadrt,writedatat,readdata);
```


```
writedata<= writedatat;
```

```
memwrite<=memwritet;
```

```
dataadr<=dataadrt;
```

```
end Behavioral;
```

## 2.RTL

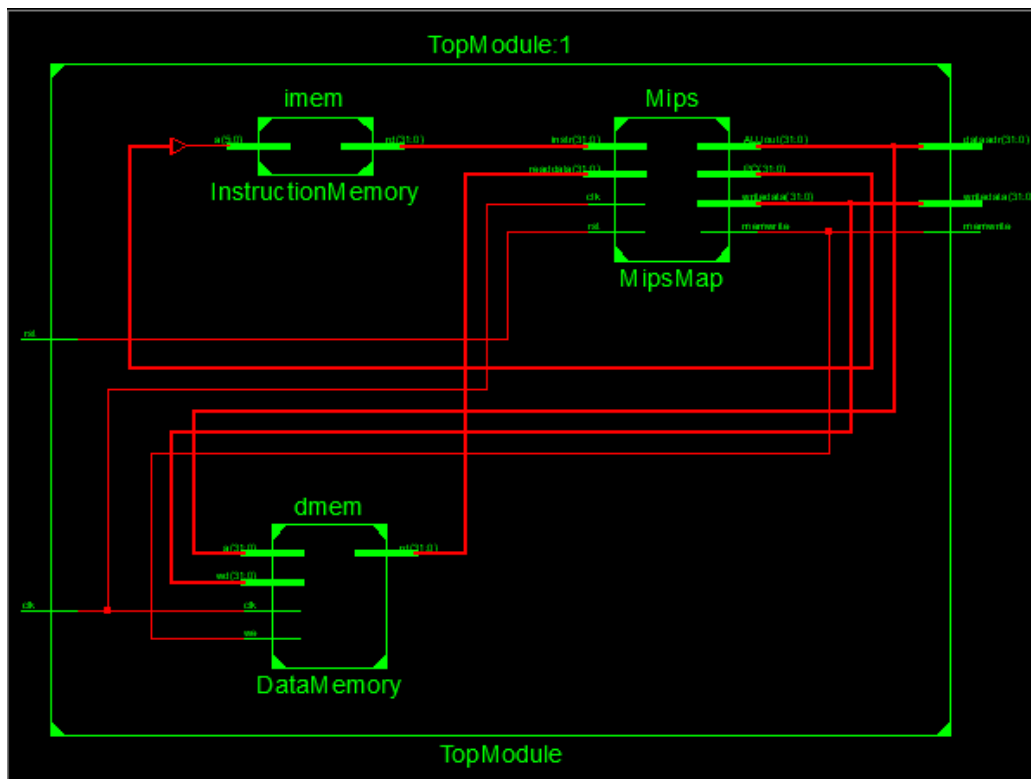



### 3. Explanation

Entity called Top Module which connect between mips, dmem and imem entities in order to test mips processor The imem module is instantiated with inputs pc(7 downto 2) and instr, The mips module is instantiated with inputs clk,reset, pc, and instr, and outputs memwritet, dataadrt, writedatat, and readdata and The dmem module is instantiated with inputs clk, memwritet, dataadrt, andwritedatat, and outputs readdata.

# MIPS

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use work.Controller_Package.all;
```

```
use work.DataPath_Package.all;
```

```
entity Mips is
```

```
    Port ( clk : in  STD_LOGIC;
```

```
          rst : in  STD_LOGIC;
```

```
          PC : out STD_LOGIC_VECTOR (31 downto 0);
```

```
          instr : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          memwrite : out STD_LOGIC;
```

```
          ALUout : out STD_LOGIC_VECTOR (31 downto 0);
```

```
          writedata : out STD_LOGIC_VECTOR (31 downto 0);
```

```
          readdata : in  STD_LOGIC_VECTOR (31 downto 0));
```

```
end Mips;
```

```
architecture Behavioral of Mips is
```

```
    signal memtoreg, alusrc, regdst, regwrite, jump, pcsrc: STD_LOGIC;
```

```
    signal zero: STD_LOGIC;
```

```
    signal alucontrol: STD_LOGIC_VECTOR (3 downto 0);
```

```
    signal pctemp,writedatatemp,aluouttemp: STD_LOGIC_VECTOR (31 downto 0);
```

```
begin
```

```
Control: controller port map(instr(31 downto 26),instr(5 downto  
0),zero,memtoreg,memwrite,pcsrc,alusrc,regdst,regwrite,jump,alucontrol);
```

```
DataP : datapath port map(clk,rst,readdata,instr,memtoreg, pcsrc,alusrc,regwrite,  
regdst,jump,alucontrol,zero,pctemp,writedata,aluouttemp);
```


```
PC <=pctemp;
```

```
writedata <= writedataTEMP;
```

```
ALUout <= aluouttemp;
```

```
end Behavioral;
```

## 2.RTL

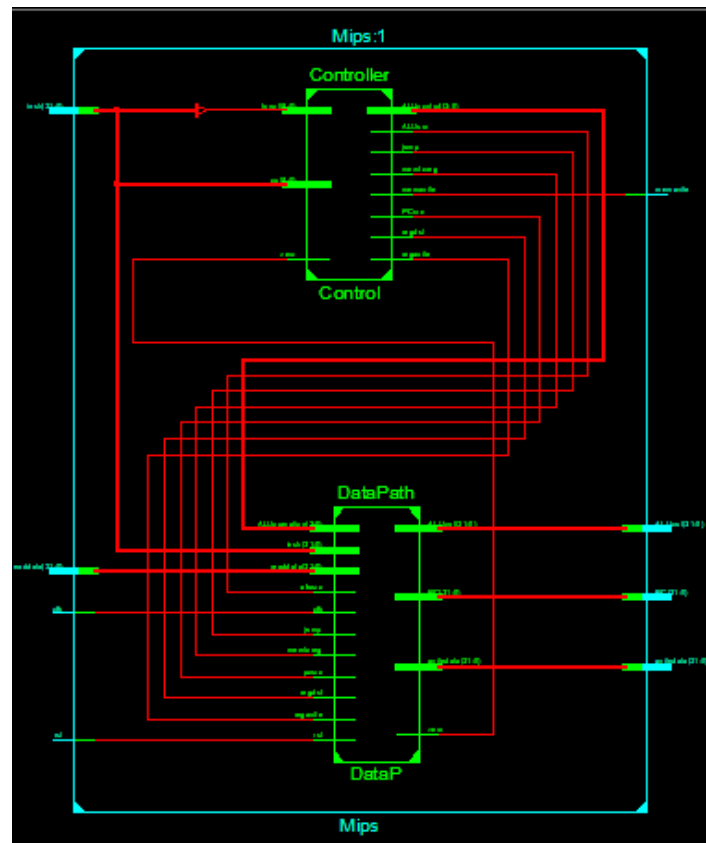

### 3.Explanation

The code provided is for an entity called "mips" which is the main module that connects the controller and datapath of a MIPS processor. The module has inputs for clock, reset, and instruction, and outputs for program counter, memory write, ALU output, write data, and read data. The control signals required for the processor are passed from the controller to the datapath using signals such as memtoreg, alusrc, regdst, regwrite, jump, pccsrc, zero, and alucontrol. This entity can be used to test the MIPS processor by instantiating it with imem and dmem entities, where imem is connected to pc(7 downto 2) and instr inputs, and dmem is connected to clk, memwrite, dataaddr, and writedata inputs, and readdata output.

# IMEM

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_SIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;
use ieee.numeric_std.all;
use IEEE.std_logic_textio.all;

library STD;
use STD.textio.all;

entity imem is -- instruction memory
port(a: in STD_LOGIC_VECTOR(5 downto 0);
rd: out STD_LOGIC_VECTOR(31 downto 0));
end;

architecture behave of imem is
begin
process is
file mem_file: TEXT;
variable L: line;
variable ch: character;
variable i, index, result: integer;
type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31 downto 0);
variable mem: ramtype;
```

```
begin
-- initialize memory from file
for i in 0 to 63 loop -- set all contents low
mem(i) := (others => '0');
end loop;
index := 0;
FILE_OPEN (mem_file, "E:/memfile.dat", READ_MODE);
while not endfile(mem_file) loop
readline(mem_file, L);
result := 0;
for i in 1 to 8 loop
read (L, ch);
if '0' <= ch and ch <= '9' then
result := character'pos(ch) - character'pos('0');
elsif 'a' <= ch and ch <= 'f' then
result := character'pos(ch) - character'pos('a')+10;
else report "Format error on line" & integer'
image(index) severity error;
end if;
mem(index)(35-i*4 downto 32-i*4):= std_logic_vector(to_unsigned(result,4));
end loop;
index := index + 1;
end loop;
-- read memory
```


```

for i in 1 to 1000 loop
  rd <= mem(CONV_INTEGER(a));
  wait on a;
end loop;
end process;

end;

```

## 2.RTL

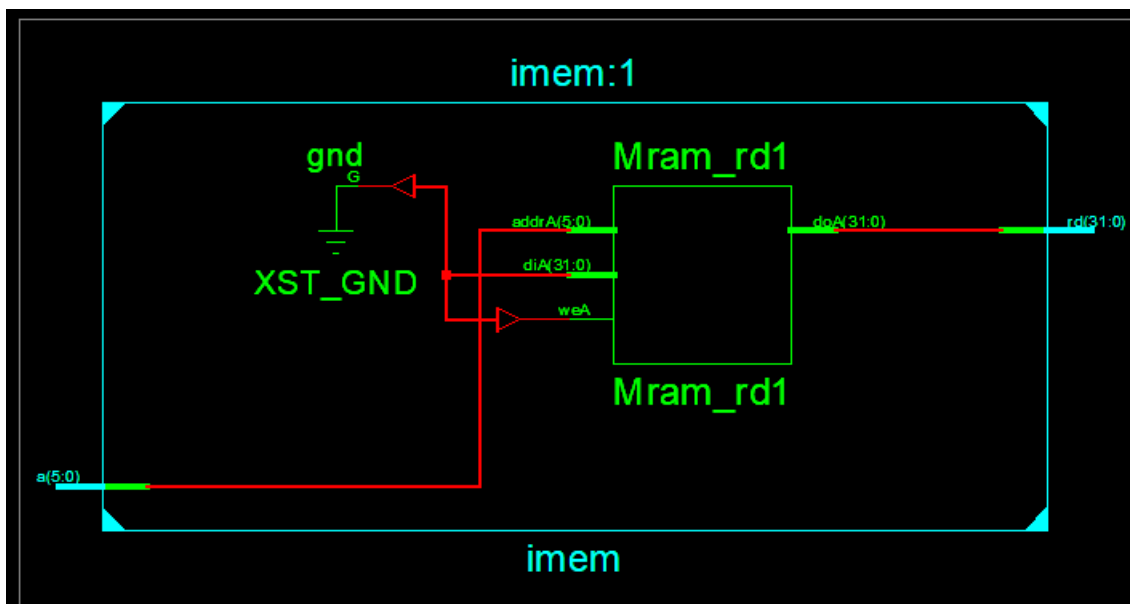

### 3.Explanation

The provided code is for an entity called "imem" which represents the instruction memory of a MIPS processor. It has one input port "a" for the address and one output port "rd" for the instruction data. The code reads the instruction memory data from a file named "memfile.dat" and stores it in a RAM-type array "mem". The entity "imem" can be used in a larger design, such as in an entity called "Main\_module" which connects between "mips", "dmem", and "imem" entities for testing the MIPS processor. The "imem" module is instantiated with inputs "pc(7 downto 2)" as the difference between instructions is 1 so we divide by 4 by skipping the first two bits as it acts like a shift right and "instr", while the "mips" module is instantiated with inputs "clk", "reset", "pc", and "instr", and outputs "memwritet", "dataadrt", "writedatat", and "readdata". Finally, the "dmem" module is instantiated with inputs "clk", "memwritet", "dataadrt", and "writedatat", and outputs "readdata".



# DMEM

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_SIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;
use ieee.numeric_std.all;

entity dmem is -- data memory
port(clk, we: in STD_LOGIC;
a, wd: in STD_LOGIC_VECTOR (31 downto 0);
rd: out STD_LOGIC_VECTOR (31 downto 0));
end;

architecture behave of dmem is
begin
process is
type ramtype is array (63 downto 0) of STD_LOGIC_VECTOR(31 downto 0);
variable mem: ramtype;
begin
-- read or write memory
for i in 1 to 1000 loop
if rising_edge(clk) then
if (we='1') then
mem (CONV_INTEGER('0'&a(7 downto 2))):= wd;
end if;

```

```

end if;

rd <= mem (CONV_INTEGER('0'&a (7 downto 2)));

wait on clk, a;


end loop;

end process;

end;

```

## 2.RTL

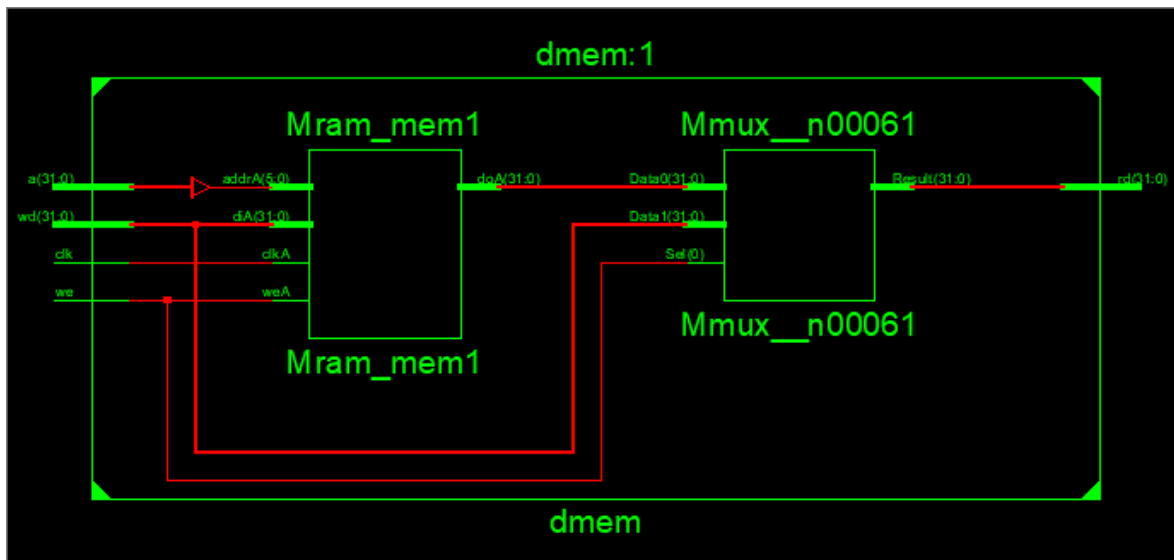

## 3.Explanation

The given code describes an entity for a data memory block that is implemented using an array of 64 words, each 32 bits wide. The memory read and write operations are synchronized using a “clk” input, with write operations controlled by the we input and data and address inputs wd and a, respectively. The output data read from the memory is provided through the “rd” output port. The memory operation is implemented in a process block, which is triggered by a rising edge of the “clk” signal. Overall, this entity describes a simple synchronous RAM block implementation for reading and writing 32-bit data values.

# Controller

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use work.ALUdecoder_Package.ALL;
```

```
use work.MainDecoder_Package.ALL;
```

entity Controller is

```
    Port ( op : in  STD_LOGIC_VECTOR (5 downto 0);
```

```
          funct : in  STD_LOGIC_VECTOR (5 downto 0);
```

```
          zero : in  STD_LOGIC;
```

```
          memtoreg : out STD_LOGIC;
```

```
          memwrite : out STD_LOGIC;
```

```
          PCsrc : out  STD_LOGIC;
```

```
          ALUsrc : out  STD_LOGIC;
```

```
          regdst : out  STD_LOGIC;
```

```
          regwrite : out STD_LOGIC;
```

```
          jump : out  STD_LOGIC;
```

```
          ALUcontrol : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end Controller;
```

architecture Behavioral of Controller is

```
    Signal ALUop : STD_LOGIC_VECTOR (1 downto 0);
```

```
    Signal branch : STD_LOGIC;
```

begin

MainDecoderMap : MainDecoder port map


(op,memtoereg,memwrite,branch,ALUsrc,regdst,regwrite,jump,ALUOp);

ALUDecoderMap : ALUdecoder port map (funct, ALUOp, ALUcontrol);

pcsrc <= branch and zero;

end Behavioral;

## 2.RTL

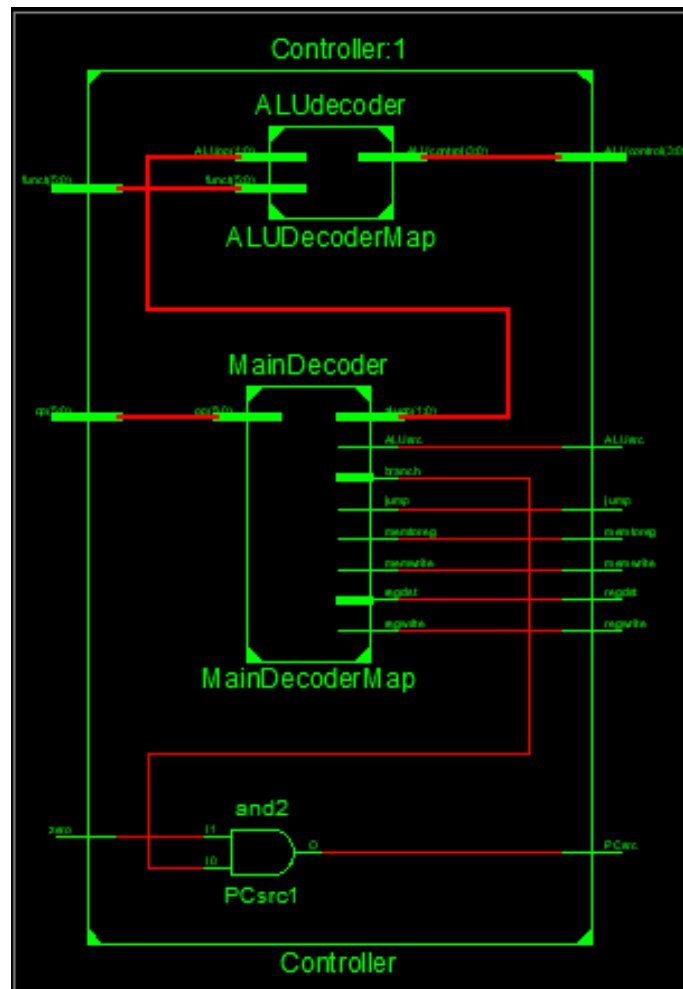

### 3. Explanation

The provided code is an implementation of a behavioral model for a controller entity in a digital circuit. The controller entity has several inputs and outputs, including op, funct, zero, memtoreg, memwrite, pcsrc, alusrc, regdst, regwrite, jump, and alucontrol. The architecture of the controller entity includes a main decoder and an ALU decoder, which decode the input signals and set the output signals. Additionally, there are signals for aluop and branch, which are used in the decoding process. The pcsrc is the branch signal **AND** Zero.

# Main Decoder

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity MainDecoder is
```

```
    Port ( op : in  STD_LOGIC_VECTOR (5 downto 0);
```

```
          memtoreg : out STD_LOGIC;
```

```
          memwrite : out STD_LOGIC;
```

```
          branch : out STD_LOGIC;
```

```
          ALUsrc : out STD_LOGIC;
```

```
          regdst : out STD_LOGIC;
```

```
          regwrite : out STD_LOGIC;
```

```
          jump : out STD_LOGIC;
```

```
          aluop : out STD_LOGIC_VECTOR (1 downto 0));
```

```
end MainDecoder;
```

```
architecture Behavioral of MainDecoder is
```

```
    signal controls: STD_LOGIC_VECTOR (8 downto 0);
```

```
begin
```

```
    process (op)
```

```
    begin
```

```
        case op is
```

```
            when "000000" => controls <="110000010"; --R type
```

```
            when "100011" => controls <="101001000"; -- lw
```

```
when "101011" => controls <= "001010000"; -- sw
when "000100" => controls <= "000100001"; -- beg
when "001000" => controls <= "101000000"; -- addi
when "000010" => controls <= "000000100"; -- j
when others => controls <= "-----"; --illegal op


end case;

end process;

(regwrite, regdst, alusrc, branch, memwrite, memtoreg, jump, aluop (1), aluop (0))
<= controls;


end Behavioral;
```

## 2.RTL

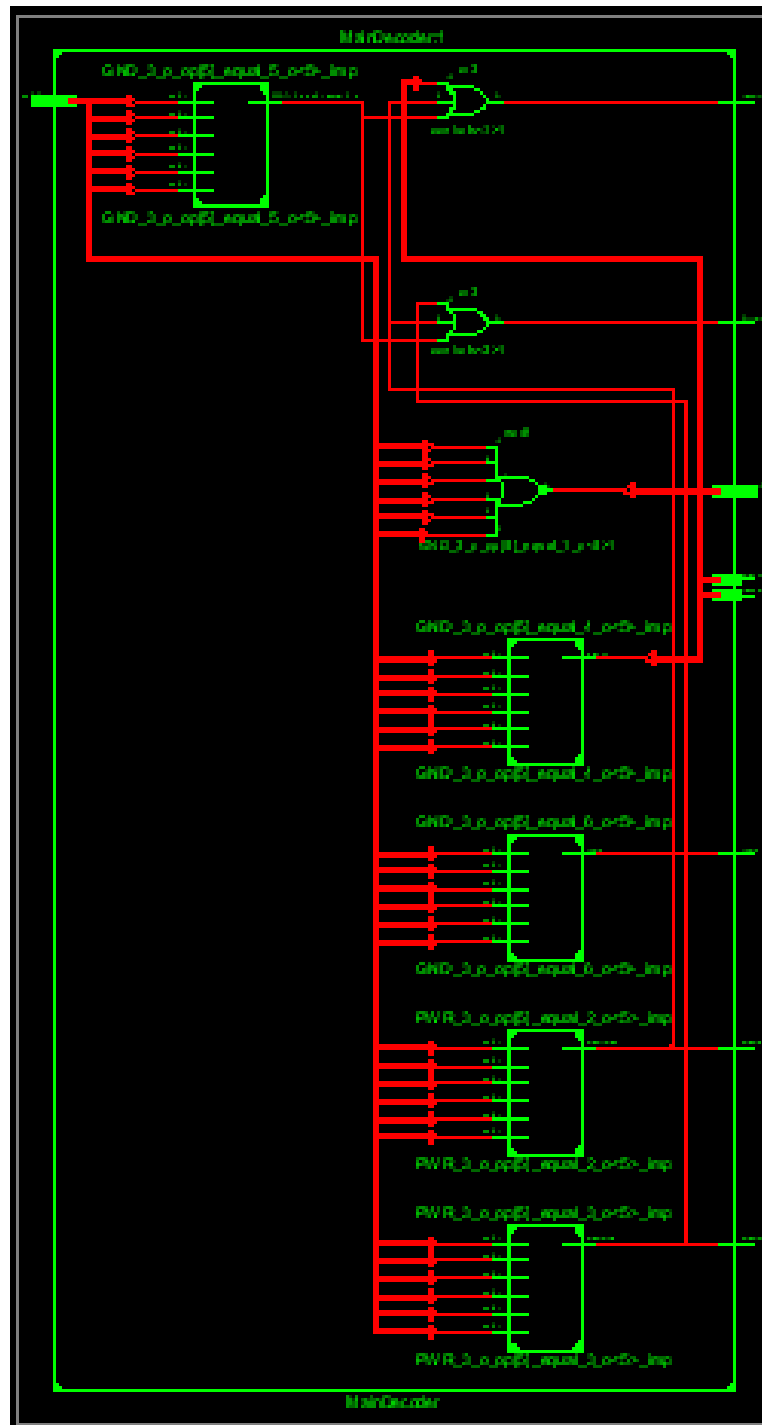



### 3.Explanation

An entity called "maindec" which takes a 6-bit input signal "op" and generates 9 control signals for a MIPS processor. The control signals include "memtoreg", "memwrite", "branch", "alusrc", "regdst", "regwrite", "jump", and "aluop" (a 2-bit signal). The entity maps the opcode of the instruction to the corresponding control signals using a case statement. The code can be used in conjunction with the imem, mips, and dmem modules to test the MIPS processor. The imem module is instantiated with inputs "pc(7 downto 2)" and "instr", the mips module is instantiated with inputs "clk", "reset", "pc", and "instr", and outputs "memwritet", "dataadrt", "writedatat", and "readdata", and the dmem module is instantiated with inputs "clk", "memwritet", "dataadrt", and "writedatat", and outputs "readdata".

# ALU Decoder

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity ALUdecoder is
```

```
    Port ( funct : in  STD_LOGIC_VECTOR (5 downto 0);
```

```
          ALUop : in  STD_LOGIC_VECTOR (1 downto 0);
```

```
          ALUcontrol : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end ALUdecoder;
```

architecture Behavioral of ALUdecoder is

```
begin
```

```
    process(ALUop,funct)
```

```
    begin
```

```
        case ALUop is
```

```
            when "00" => ALUcontrol <= "0010"; -- Add for lw/sw or addi
```

```
            when "01" => ALUcontrol <= "0110"; -- Sub for beq
```

```
            when others =>
```

```
                case funct is
```

```
                    when "100000" => ALUcontrol <= "0010"; -- Add
```

```
                    when "100010" => ALUcontrol <= "0110"; --Sub
```



### 3.Explanation

The code provided is for an entity called "aludec" which is a behavioral implementation of an ALU decoder. It has three inputs - "funct", "aluop" and one output "alucontrol". Based on the input values of "funct" and "aluop", the "alucontrol" output is determined. If "aluop" is "00" or "01", the process block sets "alucontrol" to "0010" or "0110", respectively, indicating that the ALU should perform an addition or subtraction operation. If "aluop" is neither "00" nor "01", the process block checks the "funct" signal to determine the appropriate "alucontrol" value for R-type instructions, such as add, sub, and, or, or slt. If "funct" does not match any of the R-type instructions, "alucontrol" is set to " ", indicating an unknown or unsupported operation.

# Data Path

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use work.ShiftLeft2_Package.all;

use work.Adder_Package.all;

use work.Mux2x1_Package.all;

use work.SignExtender_Package.all;

use work.ALU32_Package.all;

use work.FlopR_PKG.all;

use work.Mux32x1_Package.all;

use work.RegisterFile_Package.all;

use work.Decoder4x1_Package.all;


entity DataPath is
    Port ( clk : in  STD_LOGIC;
          rst : in  STD_LOGIC;
          readdata : in  STD_LOGIC_VECTOR (31 downto 0);
          instr : in  STD_LOGIC_VECTOR (31 downto 0);
          memtoreg, pcsrc,alusrc,regwrite, regdst,jump: in STD_LOGIC;
          ALUoperation : in  STD_LOGIC_VECTOR (3 downto 0);
          zero : out  STD_LOGIC;
          PC : buffer  STD_LOGIC_VECTOR (31 downto 0);
          writedata : buffer  STD_LOGIC_VECTOR (31 downto 0);
          ALUout : buffer  STD_LOGIC_VECTOR (31 downto 0));
```

```
end DataPath;
```

architecture Behavioral of DataPath is

```
signal wdata : STD_LOGIC_VECTOR (31 downto 0);
```

```
signal writereg: STD_LOGIC_VECTOR(4 downto 0);
```

```
signal pcjump, pcnext, pcnextbr, pcplus4, pcbranch: STD_LOGIC_VECTOR(31  
downto 0);
```

```
signal signimm, signimmsh: STD_LOGIC_VECTOR(31 downto 0);
```

```
signal srca, srcb, result: STD_LOGIC_VECTOR(31 downto 0);
```

```
signal pctemp,writedatatem,aluouttemp: STD_LOGIC_VECTOR (31 downto 0);
```

Begin

--PC

```
pcjump <= pcplus4(31 downto 28) & instr(25 downto 0) & "00";
```

```
pcreg: FlopR port map(pcnext, pctemp,clk,rst,'1');
```

```
pcadd1: Adder port map(pctemp, X"00000004", pcplus4);
```

immsh: ShiftLeft2 port map(signimm, signimmsh);

pcadd2: Adder port map(pcplus4, signimmsh, pcbranch);

pcbrmux: Mux2x1 generic map(32) port map(pcplus4, pcbranch, pcsrc, pcnextbr);

pcmux: Mux2x1 generic map(32) port map(pcnextbr, pcjump, jump, pcnext);

--Register File

-- read\_sel1

-- read\_sel2

-- write\_sel

-- write\_ena

-- clk

-- rst

-- write\_data

-- data1

-- data2

writemux: Mux2x1 generic map(5) port map(instr(20 downto 16), instr(15 downto 11), regdst, writereg);

```
RegisterFileMap : RegisterFile port map(instr(25 downto 21),instr(20 downto 16),  
writereg ,regwrite ,clk,rst,wdata,srca,writadatatemp);
```

```
resultmux: Mux2x1 generic map(32) port  
map(ALUout,readdata,memtoreg,wdata);
```

```
SignextenderMap : SignExtender port map(instr(15 downto 0),signimm);
```

```
--ALU
```

```
srcbmux: Mux2x1 generic map(32) port map(writadatatemp,signimm,alusrc,srcb);
```

```
AluMap : ALU32 port map (srca,srcb,ALUoperation,aluouttemp,zero);
```

```
pc <= ptemp;
```


```
writedata <= writadatatemp;
```

```
ALUout <= aluouttemp;
```

```
end Behavioral;
```



## 2.RTL

 

## 3.Explanation

This is code for a datapath module that includes a PC, register file, and ALU. The module has several input and output ports such as clk, reset, readdata, instr, memtoreg, pcsrc, alusrc, regwrite, regdst, jump, aluoperation, zero, pc, writedata, and aluout. The code includes signals for data manipulation, and several sub-components like a flopr, adder, mux, and signextender. The PC section is responsible for updating the program counter based on different conditions, while the register file reads and writes data to registers. The ALU performs arithmetic and logic operations on data coming from the register file or the signextender. The outputs of the datapath module are the updated PC value, data to be written to memory or register file, and the output of the ALU.

# Register File

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

use IEEE.STD_LOGIC_unsigned.ALL;


use work.Decoder4x1_Package.all;
use work.FlopR_PKG.all;
use work.ALU32_Package.all;
use work.Mux32x1_Package.all;


entity RegisterFile is
    Port ( read_sel1 : in  STD_LOGIC_VECTOR (4 downto 0);
          read_sel2 : in  STD_LOGIC_VECTOR (4 downto 0);
          write_sel : in  STD_LOGIC_VECTOR (4 downto 0);
          write_ena : in  STD_LOGIC;
          clk : in  STD_LOGIC;
          rst : in  STD_LOGIC;
          write_data : in  STD_LOGIC_VECTOR (31 downto 0);
          data1 : out  STD_LOGIC_VECTOR (31 downto 0);
          data2 : out  STD_LOGIC_VECTOR (31 downto 0));
end RegisterFile;
```

architecture Behavioral of RegisterFile is

--Decoder signal

signal Decoderout: STD\_LOGIC\_VECTOR (31 downto 0);

--Register signals

signal sig1 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig2 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig3 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig4 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig5 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig6 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig7 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig8 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig9 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig10 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig11 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig12 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig13 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig14 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig15 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig16 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig17 : STD\_LOGIC\_VECTOR(31 downto 0);

signal sig18 : STD\_LOGIC\_VECTOR(31 downto 0);

```
signal sig19 : STD_LOGIC_VECTOR(31 downto 0);
signal sig20 : STD_LOGIC_VECTOR(31 downto 0);
signal sig21 : STD_LOGIC_VECTOR(31 downto 0);
signal sig22 : STD_LOGIC_VECTOR(31 downto 0);
signal sig23 : STD_LOGIC_VECTOR(31 downto 0);
signal sig24 : STD_LOGIC_VECTOR(31 downto 0);
signal sig25 : STD_LOGIC_VECTOR(31 downto 0);
signal sig26 : STD_LOGIC_VECTOR(31 downto 0);
signal sig27 : STD_LOGIC_VECTOR(31 downto 0);
signal sig28 : STD_LOGIC_VECTOR(31 downto 0);
signal sig29 : STD_LOGIC_VECTOR(31 downto 0);
signal sig30 : STD_LOGIC_VECTOR(31 downto 0);
signal sig31 : STD_LOGIC_VECTOR(31 downto 0);
signal sig32 : STD_LOGIC_VECTOR(31 downto 0);
```

```
begin
```

```
--Decoder Implement
```

```
--I,O
```

```
DecoderMap : Decoder4x1 port map(write_sel,DecoderOut);
```

```
--FlopR Implement
```

```
--D,Q,Clock,Rst, wr_en
```

flopRMap1: FlopR port map(write\_data, sig1, Clk, rst, write\_ena and Decoderout(0));

flopRMap2: FlopR port map(write\_data, sig2, Clk, rst, write\_ena and Decoderout(1));

flopRMap3: FlopR port map(write\_data, sig3, Clk, rst, write\_ena and Decoderout(2));

flopRMap4: FlopR port map(write\_data, sig4, Clk, rst, write\_ena and Decoderout(3));

flopRMap5: FlopR port map(write\_data, sig5, Clk, rst, write\_ena and Decoderout(4));

flopRMap6: FlopR port map(write\_data, sig6, Clk, rst, write\_ena and Decoderout(5));

flopRMap7: FlopR port map(write\_data, sig7, Clk, rst, write\_ena and Decoderout(6));

flopRMap8: FlopR port map(write\_data, sig8, Clk, rst, write\_ena and Decoderout(7));

flopRMap9: FlopR port map(write\_data, sig9, Clk, rst, write\_ena and Decoderout(8));

flopRMap10: FlopR port map(write\_data, sig10, Clk, rst, write\_ena and Decoderout(9));

flopRMap11: FlopR port map(write\_data, sig11, Clk, rst, write\_ena and Decoderout(10));

flopRMap12: FlopR port map(write\_data, sig12, Clk, rst, write\_ena and Decoderout(11));

flopRMap13: FlopR port map(write\_data, sig13, Clk, rst, write\_ena and Decoderout(12));

flopRMap14: FlopR port map(write\_data, sig14, Clk, rst, write\_ena and Decoderout(13));

flopRMap15: FlopR port map(write\_data, sig15, Clk, rst, write\_ena and Decoderout(14));

flopRMap16: FlopR port map(write\_data, sig16, Clk, rst, write\_ena and Decoderout(15));

flopRMap17: FlopR port map(write\_data, sig17, Clk, rst, write\_ena and Decoderout(16));

flopRMap18: FlopR port map(write\_data, sig18, Clk, rst, write\_ena and Decoderout(17));

flopRMap19: FlopR port map(write\_data, sig19, Clk, rst, write\_ena and Decoderout(18));

flopRMap20: FlopR port map(write\_data, sig20, Clk, rst, write\_ena and Decoderout(19));

flopRMap21: FlopR port map(write\_data, sig21, Clk, rst, write\_ena and Decoderout(20));

flopRMap22: FlopR port map(write\_data, sig22, Clk, rst, write\_ena and Decoderout(21));

flopRMap23: FlopR port map(write\_data, sig23, Clk, rst, write\_ena and Decoderout(22));

flopRMap24: FlopR port map(write\_data, sig24, Clk, rst, write\_ena and Decoderout(23));

flopRMap25: FlopR port map(write\_data, sig25, Clk, rst, write\_ena and Decoderout(24));

flopRMap26: FlopR port map(write\_data, sig26, Clk, rst, write\_ena and Decoderout(25));

flopRMap27: FlopR port map(write\_data, sig27, Clk, rst, write\_ena and Decoderout(26));

flopRMap28: FlopR port map(write\_data, sig28, Clk, rst, write\_ena and Decoderout(27));

flopRMap29: FlopR port map(write\_data, sig29, Clk, rst, write\_ena and Decoderout(28));

flopRMap30: FlopR port map(write\_data, sig30, Clk, rst, write\_ena and Decoderout(29));

flopRMap31: FlopR port map(write\_data, sig31, Clk, rst, write\_ena and Decoderout(30));

flopRMap32: FlopR port map(write\_data, sig32, Clk, rst, write\_ena and Decoderout(31));

--Mux 1

--signal 1-32,Selector,Output

Mux1Map : Mux32x1 port map(


sig1, sig2, sig3, sig4, sig5, sig6, sig7, sig8,  
sig9, sig10, sig11, sig12, sig13, sig14, sig15, sig16,  
sig17, sig18, sig19, sig20, sig21, sig22, sig23, sig24,  
sig25, sig26, sig27, sig28, sig29, sig30, sig31, sig32,  
read\_sel1, data1);

Mux2Map : Mux32x1 port map(


sig1, sig2, sig3, sig4, sig5, sig6, sig7, sig8,  
sig9, sig10, sig11, sig12, sig13, sig14, sig15, sig16,  
sig17, sig18, sig19, sig20, sig21, sig22, sig23, sig24,  
sig25, sig26, sig27, sig28, sig29, sig30, sig31, sig32,  
read\_sel2, data2);


end Behavioral;

## 2.RTL

 



 

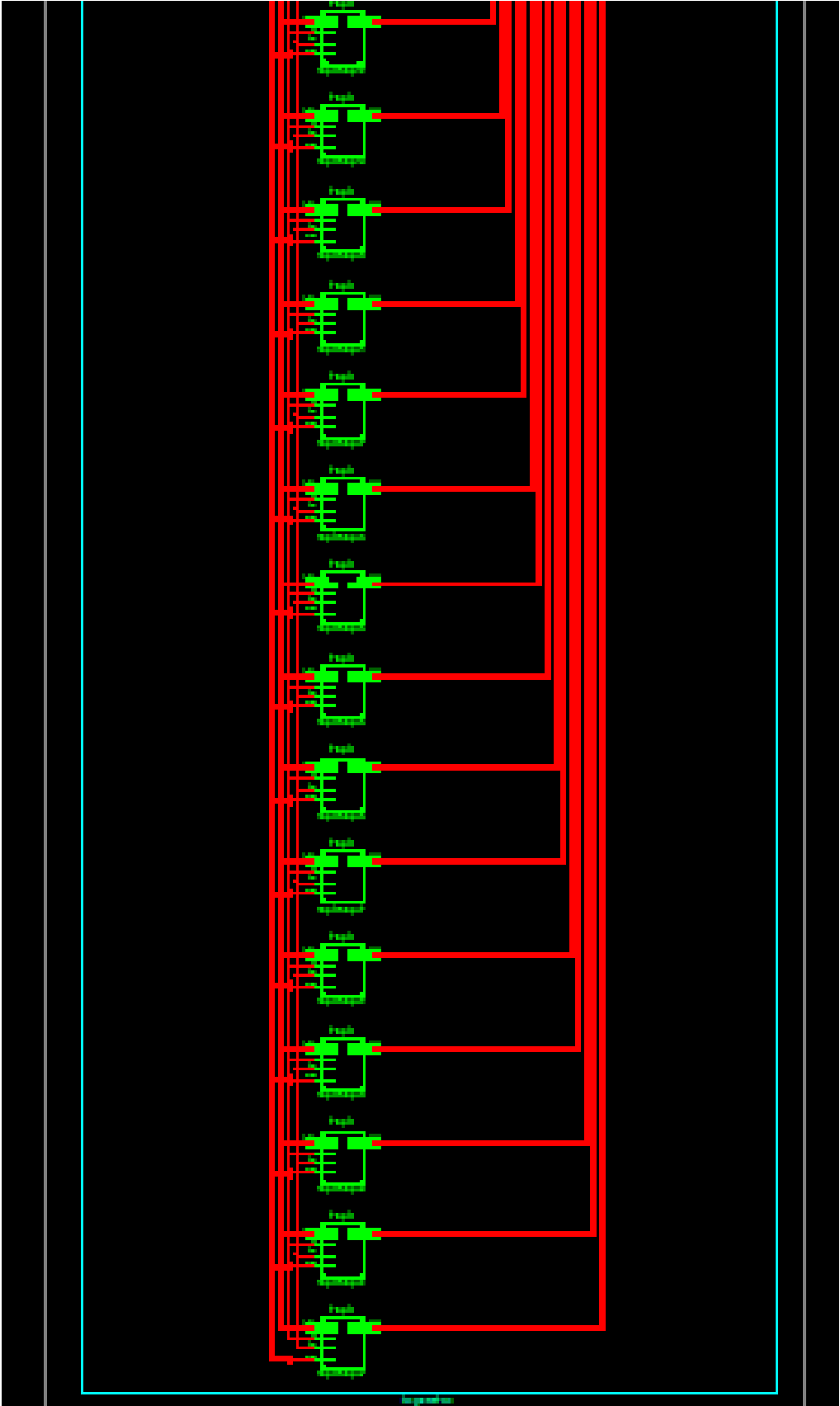

### 3.Explanation

The register file has 32 registers each of 32-bit width. The register file has two read ports and one write port. The register file is asynchronous reset and positive-edge clock-triggered.

The module RegFile has the following ports:

- read\_sel1, read\_sel2: 5-bit input ports that are used to select the registers to be read from.
- write\_sel: 5-bit input port that is used to select the register to be written to.
- write\_ena: 1-bit input port that is used to enable/disable writing to the selected register.
- clk, reset: input ports for clock and reset signals respectively.
- write\_data: 32-bit input port that provides data to be written to the selected register.
- data1, data2: 32-bit output ports that provide the data read from the selected registers

# ALU

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
use IEEE.STD_LOGIC_unsigned.ALL;
```

```
entity ALU32 is
```

```
    Port ( data1 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          data2 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          aluop  : in  STD_LOGIC_VECTOR (3 downto 0);
```

```
          dataout : out STD_LOGIC_VECTOR (31 downto 0);
```

```
          zflag  : out STD_LOGIC);
```

```
end ALU32;
```

```
architecture Behavioral of ALU32 is
```

```
    signal result: STD_LOGIC_VECTOR (31 downto 0);
```

```
    signal slt: STD_LOGIC_VECTOR (31 downto 0);
```

```
    signal temp: STD_LOGIC_VECTOR (32 downto 0);
```

```
begin
```

```
    temp <= (('0' & data1) + ('0' & data2)) WHEN aluop = "0010" ELSE
```

```
    (('0' & data1) - ('0' & data2)) WHEN aluop = "0110" ELSE
```

```
    (OTHERS=>'0');
```

```

slt <= X"00000001" WHEN data1 < data2 ELSE
X"00000000";

result <= data1 AND data2 when aluop = "0000" ELSE
data1 OR data2 when aluop = "0001" ELSE
temp(31 downto 0) when aluop = "0010" ELSE
temp(31 downto 0) when aluop = "0110" ELSE
data1 NOR data2 when aluop = "1100" ELSE
slt when aluop = "0111";


zflag <= '1' when result = X"00000000" ELSE
'0';



dataout <= result;



end Behavioral;

```

## 2.RTL

 

 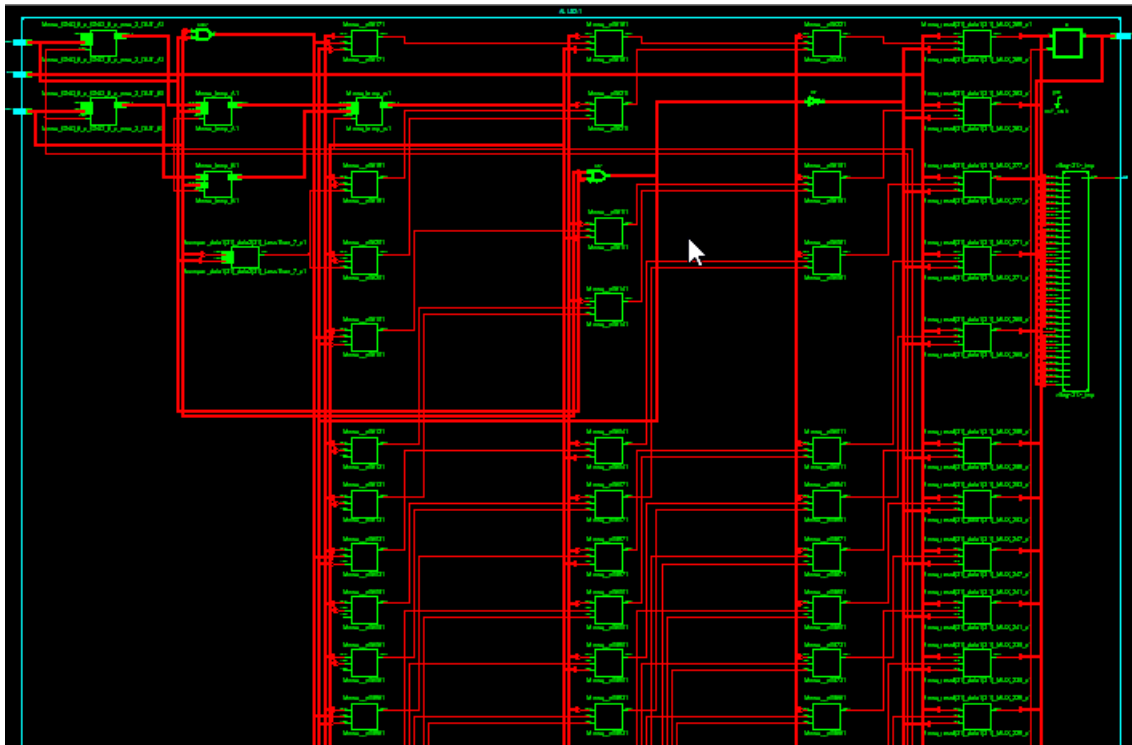

  

### 3.Explanation

An ALU (Arithmetic Logic Unit) module that performs various arithmetic and logic operations on two 32-bit input data (data1 and data2) based on a 4-bit operation code (aluop) and produces a 32-bit output (dataout) and a zero flag (zflag).



# Mux 2\*1

## 1.Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux2x1 is
    generic(width: integer);
    Port ( A,B : in  STD_LOGIC_VECTOR (width-1 downto 0);
          S : in  STD_LOGIC;
          O : out STD_LOGIC_VECTOR (width-1 downto 0));
end Mux2x1;

architecture Behavioral of Mux2x1 is

begin

    O <= B when S = '1' else A;

end Behavioral;
```

# Mux 32\*1

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Mux32x1 is
```

```
    Port ( i1 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i2 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i3 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i4 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i5 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i6 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i7 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i8 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i9 : in  STD_LOGIC_VECTOR (31 downto 0);
```

```
          i10 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i11 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i12 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i13 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i14 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i15 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i16 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i17 : in STD_LOGIC_VECTOR (31 downto 0);
```

```
          i18 : in STD_LOGIC_VECTOR (31 downto 0);
```

```

i19 : in STD_LOGIC_VECTOR (31 downto 0);
i20 : in STD_LOGIC_VECTOR (31 downto 0);
i21 : in STD_LOGIC_VECTOR (31 downto 0);
i22 : in STD_LOGIC_VECTOR (31 downto 0);
i23 : in STD_LOGIC_VECTOR (31 downto 0);
i24 : in STD_LOGIC_VECTOR (31 downto 0);
i25 : in STD_LOGIC_VECTOR (31 downto 0);
i26 : in STD_LOGIC_VECTOR (31 downto 0);
i27 : in STD_LOGIC_VECTOR (31 downto 0);
i28 : in STD_LOGIC_VECTOR (31 downto 0);
i29 : in STD_LOGIC_VECTOR (31 downto 0);
i30 : in STD_LOGIC_VECTOR (31 downto 0);
i31 : in STD_LOGIC_VECTOR (31 downto 0);
i32 : in STD_LOGIC_VECTOR (31 downto 0);
S : in STD_LOGIC_VECTOR (4 downto 0);
O : out STD_LOGIC_VECTOR (31 downto 0));
end Mux32x1;

```

architecture Behavioral of Mux32x1 is

```
begin
```

```
    o <=
```

```
    i1 when s="00000" else
```

```
    i2 when s="00001" else

```

i3 when s="00010"else  
i4 when s="00011"else  
i5 when s="00100"else  
i6 when s="00101"else  
i7 when s="00110"else  
i8 when s="00111"else  
i9 when s="01000"else  
i10 when s="01001"else  
i11 when s="01010"else  
i12 when s="01011"else  
i13 when s="01100"else  
i14 when s="01101"else  
i15 when s="01110"else  
i16 when s="01111"else  
i17 when s="10000"else  
i18 when s="10001"else  
i19 when s="10010"else  
i20 when s="10011"else  
i21 when s="10100"else  
i22 when s="10101"else  
i23 when s="10110"else  
i24 when s="10111"else  
i25 when s="11000"else  
i26 when s="11001"else

end Behavioral;

[illegible]

# Flopr

## 1.Code

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_unsigned.all;
```

entity FlopR is

```
    Port ( D : in  STD_LOGIC_VECTOR (31 downto 0);  
          Q : out STD_LOGIC_VECTOR (31 downto 0);  
          Clk : in  STD_LOGIC;  
          Rst : in  STD_LOGIC;  
          wr_en: in STD_LOGIC);
```

end FlopR;

--D,Q,Clk,Rst

architecture Behavioral of FlopR is

begin

PROCESS(Clk,rst)

Begin

IF(rst='1') THEN

```
    Q <=(others => '0');
```

```
ELSIF (Clk'EVENT and clk = '1' and wr_en = '1') THEN
```


```
    Q <= D;
```

```
END IF;
```

```
END PROCESS;
```

```
end Behavioral;
```

## 2.RTL

 

## Decoder

## 1.Code

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity Decoder4x1 is

```
Port ( I : in STD_LOGIC_VECTOR (4 downto 0);
```

```
O : out STD_LOGIC_VECTOR (31 downto 0));
```

```
end Decoder4x1;
```

### architecture Behavioral of Decoder4x1 is

begin

 $0 \leq$ 

```
"000000000000000000000000000000000001" when l = "00000" else
```

```
"00000000000000000000000000000000010" when l = "00001" else
```

```
"0000000000000000000000000000000000100" when l = "00010" else
```


[illegible][illegible][illegible][illegible][illegible][illegible][illegible]



[illegible]

end Behavioral;

## 2.RTL

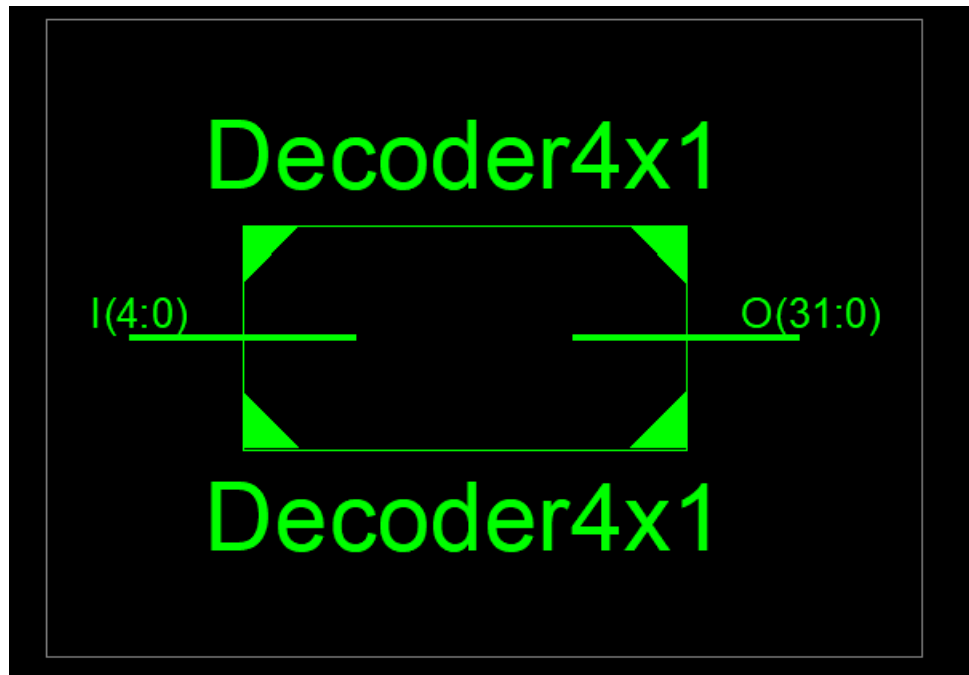

# Adder

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Adder is
    Port ( A : in  STD_LOGIC_VECTOR (31 downto 0);
          B : in  STD_LOGIC_VECTOR (31 downto 0);
          O : out STD_LOGIC_VECTOR (31 downto 0));
end Adder;


architecture Behavioral of Adder is

begin

    O <= A+B;

end Behavioral;
```

## 2.RTL

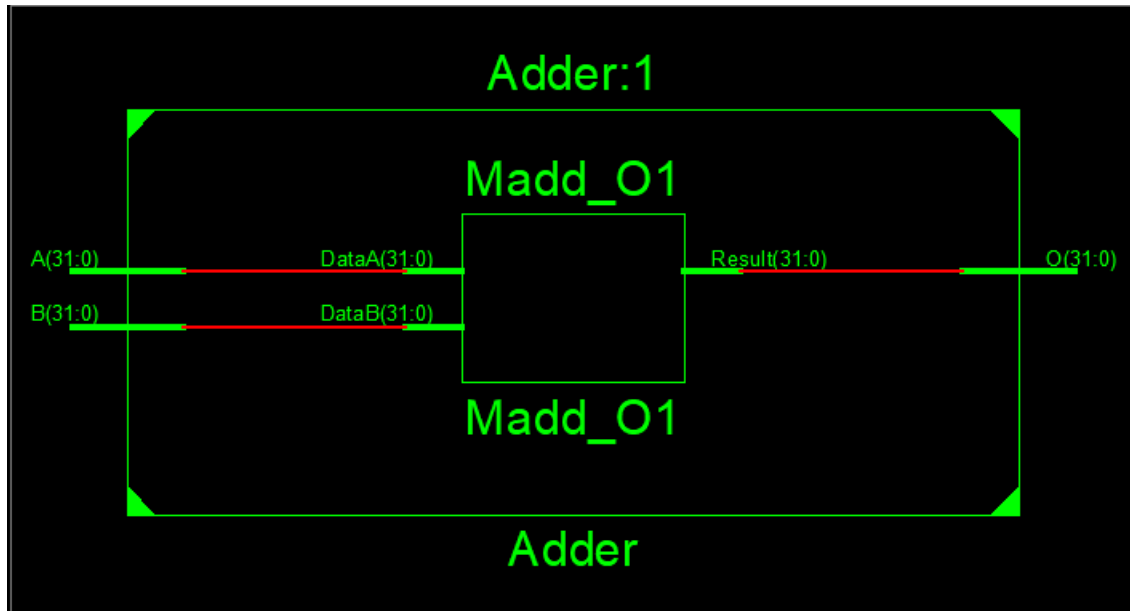

# Sign Extender

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity SignExtender is
    Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
          O : out STD_LOGIC_VECTOR (31 downto 0));
end SignExtender;


architecture Behavioral of SignExtender is

begin

    O <= X"ffff" & A when A(15) = '1' else X"0000" & A;

end Behavioral;
```

## 2.RTL

 

# Shift left 2

## 1.Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity ShiftLeft2 is

    Port ( A : in  STD_LOGIC_VECTOR (31 downto 0);

          O : out STD_LOGIC_VECTOR (31 downto 0));

end ShiftLeft2;


architecture Behavioral of ShiftLeft2 is

begin

    O <= A(29 downto 0) & "00";

end Behavioral;
```

## 2.RTL

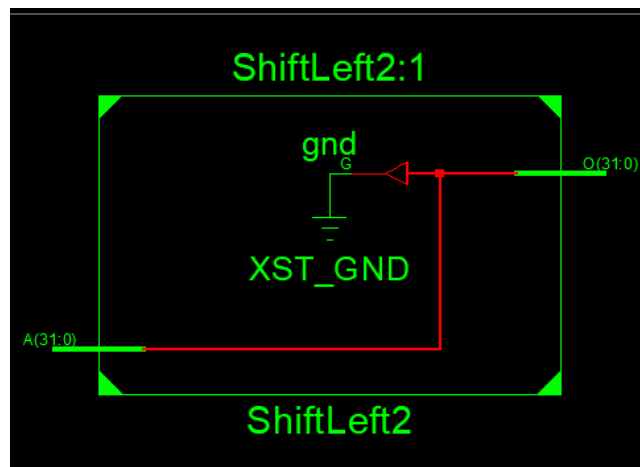

# Test Files

## Main Module Test

### 1. Code

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_SIGNED.all;
use IEEE.STD_LOGIC_ARITH.all;
use ieee.numeric_std.all;
-- use IEEE.NUMERIC_STD_UNSIGNED.all;

entity testbench is
end;

architecture test of testbench is
    component TopModule
        port(clk, rst: in STD_LOGIC;
            writedata, dataadr: out STD_LOGIC_VECTOR(31 downto 0);
            memwrite: out STD_LOGIC);
    end component;
    signal writedata, dataadr: STD_LOGIC_VECTOR(31 downto 0);
    signal clk, reset, memwrite: STD_LOGIC;

begin
    -- instantiate device to be tested
    dut: TopModule port map(clk, reset, writedata, dataadr, memwrite);
```

-- Generate clock with 10 ns period

process begin

clk <= '1';

wait for 5 ns;

clk <= '0';

wait for 5 ns;

end process;

-- Generate reset for first two clock cycles

process begin

reset <= '1';

wait for 22 ns;

reset <= '0';

wait;

end process;

-- check that 7 gets written to address 84 at end of program

process(clk) begin

if (clk'event and clk = '0' and memwrite = '1') then

if (CONV\_INTEGER(dataadr) = 84 and CONV\_INTEGER(writedata) = 7) then

report "NO ERRORS: Simulation succeeded" severity failure;

elsif (CONV\_INTEGER(dataadr) = 84) then

report "Simulation failed" severity failure;



end if;

end if;

end process;

end;

## 2.Test Results

